 


Lab Two

Verilog



Waleed Emad Yahyaa Zakarya

BINARY TO GRAY

```
module binary_gray_behavioral (binary,gray);

/*input output declaration of port list*/
input wire [2:0] binary;
output reg [2:0] gray;

/*behavioral code for describing the binary to gray code using case*/
always @(*) begin
    case (binary)
        3'b000: gray = 3'b000;
        3'b001: gray = 3'b001;
        3'b010: gray = 3'b011;
        3'b011: gray = 3'b010;
        3'b100: gray = 3'b110;
        3'b101: gray = 3'b111;
        3'b110: gray = 3'b101;
        3'b111: gray = 3'b100;
    endcase
end

endmodule
```

```
module binary_gray_behavioral_TB ( );


/*internal variables for using in test bench*/
reg [2:0] binaryTB;
wire [2:0] grayTB;
integer i = 0;

/*instantioation of main module*/
binary_gray_behavioral TBinstance(binaryTB,grayTB);

/*appling all possible stimulas*/
initial begin
    $monitor ("binary = %b _____ gray = %b",binaryTB,grayTB);
    for (i=0;i<8;i=i+1)
        #5 binaryTB = i;
end

endmodule
```

```
# Compile of GrayCodeTB.v was successful.
VSIM 26> restart
# ** Note: (vsim-3813) Design is being optimized due to module recompilation...
# Loading work.binary_gray_behavioral_TB(fast)
# Loading work.binary_gray_behavioral(fast)
VSIM 27> run
# binary = xxx      gray = xxx
# binary = 000      gray = 000
# binary = 001      gray = 001
# binary = 010      gray = 011
# binary = 011      gray = 010
# binary = 100      gray = 110
# binary = 101      gray = 111
# binary = 110      gray = 101
# binary = 111      gray = 100
```

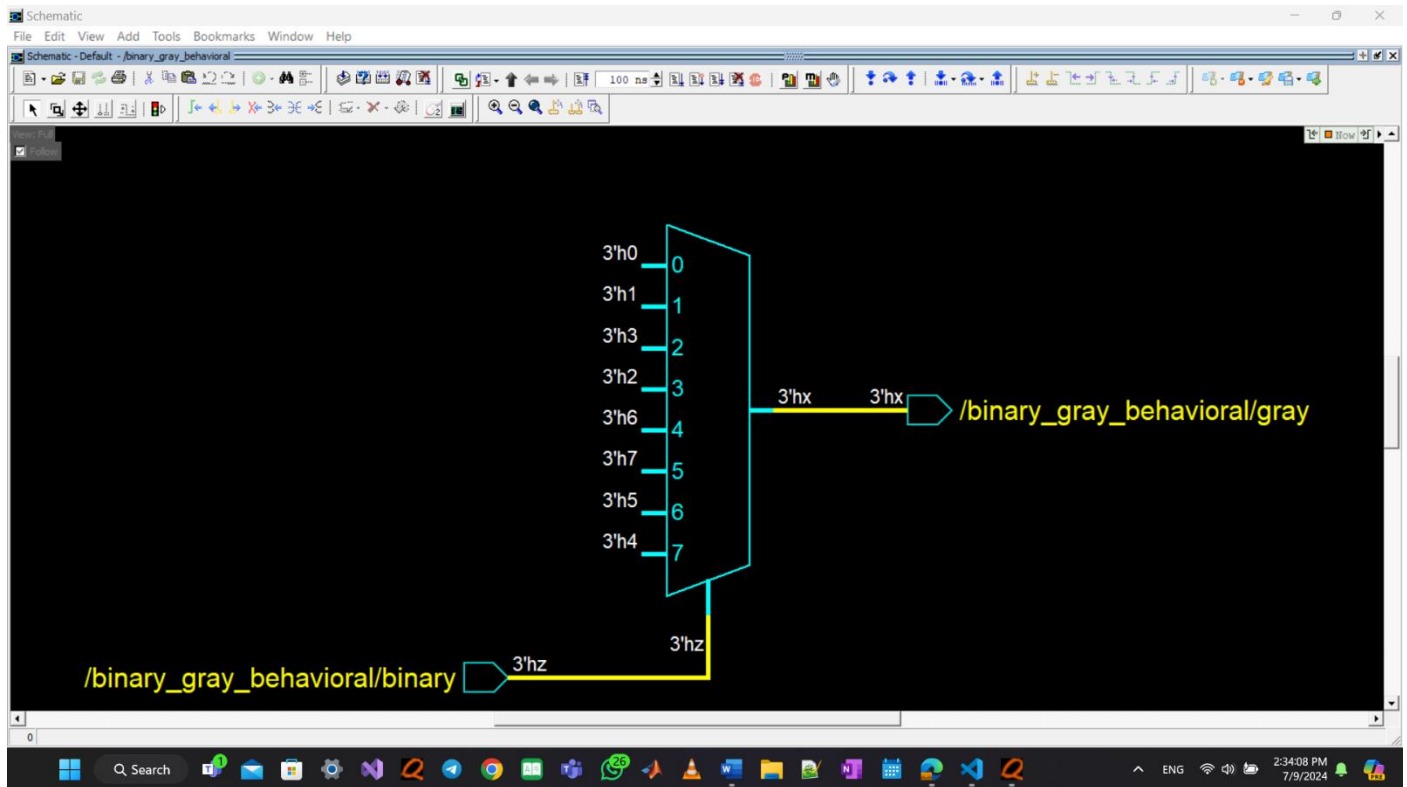

4-BIT PISO (PARALLEL TO SERIAL)

```

module piso (clk,rst,sel,indata,outbit);

input wire clk , rst , sel;
input wire [3:0] indata;
output reg outbit;

reg [3:0] internalreg;

always @(posedge clk )
begin
    if (rst)
    begin
        internalreg <= 4'b000;
        outbit <=0;
    end
    else if (sel == 1'b0)
    begin
        internalreg <= indata;
    end
    else if (sel == 1'b1)
    begin
        outbit <= internalreg[0];
        internalreg[3:0] <= {1'b0,{internalreg[3:1]}};
    end
    else
    begin
        outbit <= 1'b0;
    end
end
endmodule

```

[illegible]

 Schematic

4-BIT SIPO (SERIAL TO PARALLEL)

```
module sipo (clk,rst,inbit,outdata);

parameter N = 4;

input wire clk , rst , inbit;
output reg [N-1:0] outdata;

integer i;

always @(negedge clk)
begin
    if (rst)
        begin
            outdata <= 0;
        end
    else
        begin
            outdata <= {inbit,{outdata[N-1:1]}};
        end
    end
end

endmodule

module sipo_TB ( );

reg clk_TB , rst_TB , inbit_TB;
wire [3:0] outdata_TB;

integer i = 0;

sipo sipo_TB_instance (clk_TB,rst_TB,inbit_TB,outdata_TB);

initial
begin
    clk_TB = 0;
    forever #5 clk_TB = ~clk_TB;
end

initial begin
    $monitor ("time = %0t _____ datain = %b _____ dataout = %b", $time, inbit_TB, outdata_TB);
    rst_TB = 0;
    #20 rst_TB = 1;
    #20 rst_TB = 0;
    inbit_TB = 0;
    for (i=0;i<8;i=i+1)
        #20 inbit_TB = ~inbit_TB;
end

endmodule
```



```
C: predict <= 0;
```

```

D: predict <= 0;
endcase
end

always @(posedge clk)
begin
    case (curr_state)
    A:
        begin
            if (taken == 0)
                nxt_state <= B;
            else if (taken == 1)
                nxt_state <= A;
            else
                nxt_state <= A;
        end
    B:
        begin
            if (taken == 0)
                nxt_state <= C;
            else if (taken == 1)
                nxt_state <= A;
            else
                nxt_state <= A;
        end
    C:
        begin
            if (taken == 0)
                nxt_state <= C;
            else if (taken == 1)
                nxt_state <= D;
            else
                nxt_state <= A;
        end
    D:
        begin
            if (taken == 0)
                nxt_state <= C;
            else if (taken == 1)
                nxt_state <= A;
            else
                nxt_state <= A;
        end
    endcase
end

endmodule

module predict_TB ();

reg rst_TB , clk_TB = 1'b0 , taken_TB ;
wire predict_TB ;

predict predict_instance (rst_TB , clk_TB , taken_TB , predict_TB);

```



```
always #5 clk_TB = ~clk_TB;
```

```
initial begin
```

```
$monitor("rst_TB = %b , clk_TB = %b , taken_TB = %b , predict_TB = %b",rst_TB , clk_TB ,  
taken_TB , predict_TB);
```

```
rst_TB=0; taken_TB=0;
```

```
#20 rst_TB = 1;
```

```
#20 rst_TB = 0;
```

```
#20 rst_TB = 1;
```

```
#2 taken_TB=1;
```

```
#10 taken_TB=1;
```

```
#10 taken_TB=0;
```

```
#10 taken_TB=1;
```

```
#10 taken_TB=0;
```

```
#10 taken_TB=0;
```

```
#10 taken_TB=1;
```

```
#10 taken_TB=1;
```

```
#10 taken_TB=1;
```

```
#10 taken_TB=0;
```

```
#10 taken_TB=0;
```


```
#10 taken_TB=1;
```

```
#10 taken_TB=1;
```

```
end
```

```
endmodule
```

```
# clk=0 ,rst=0 ,sel=1 ,indata=0000 ,outbit=x  
# clk=1 ,rst=0 ,sel=1 ,indata=0000 ,outbit=x  
# clk=0 ,rst=0 ,sel=1 ,indata=0000 ,outbit=x  
# clk=1 ,rst=0 ,sel=1 ,indata=0000 ,outbit=x  
# clk=0 ,rst=1 ,sel=1 ,indata=0000 ,outbit=x  
# clk=1 ,rst=1 ,sel=1 ,indata=0000 ,outbit=0  
# clk=0 ,rst=1 ,sel=1 ,indata=0000 ,outbit=0  
# clk=1 ,rst=1 ,sel=1 ,indata=0000 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0000 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0000 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0000 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0000 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=0 ,rst=0 ,sel=0 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=0 ,indata=0101 ,outbit=0  
# clk=0 ,rst=0 ,sel=0 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=0 ,indata=0101 ,outbit=0  
VSIW 27> run  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=1  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=1  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=1  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=1  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=0 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0  
# clk=1 ,rst=0 ,sel=1 ,indata=0101 ,outbit=0
```

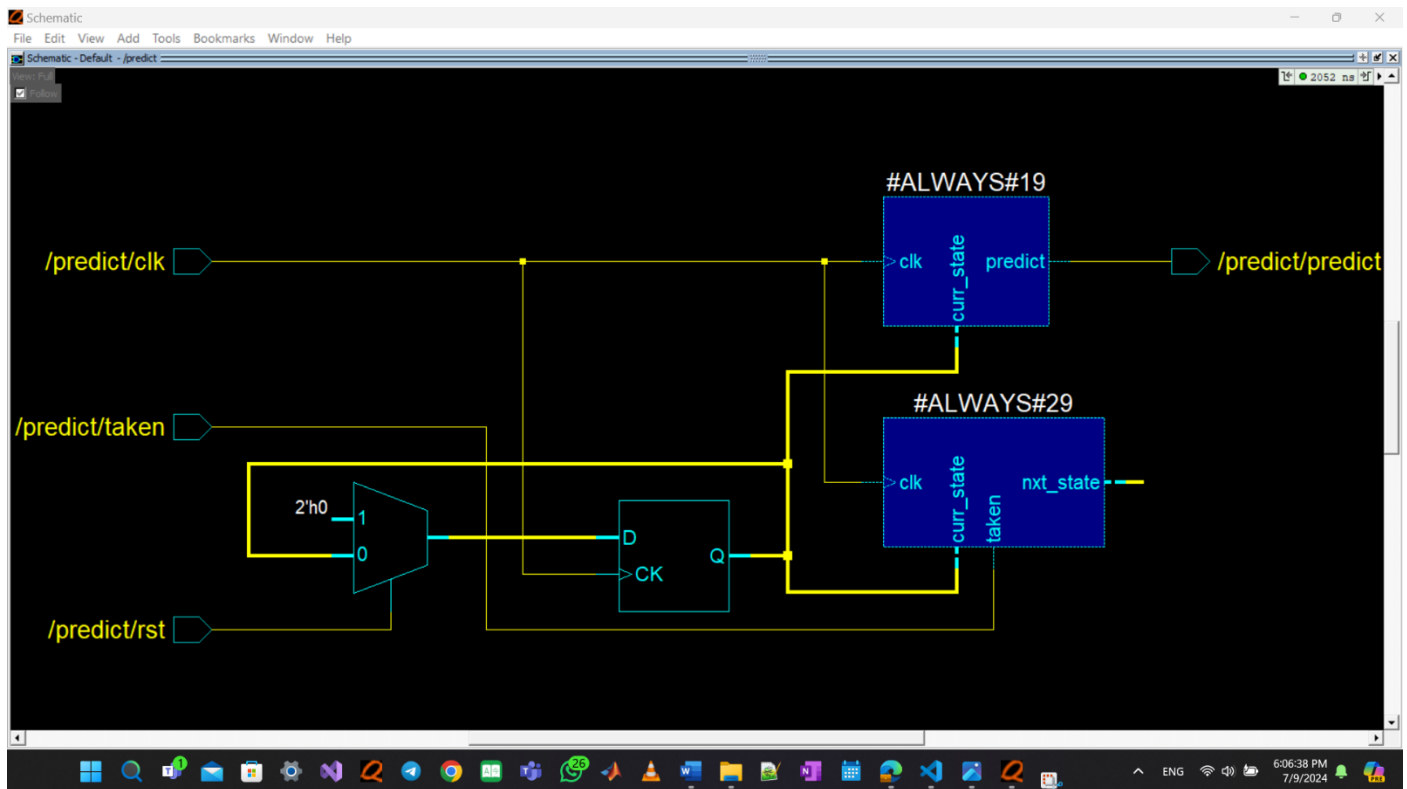

SEQUENCE DETECTOR

```

module seq_dete_method1 (
    input rst,clk,datain,
    output reg dataout );

localparam A = 0,
           B = 1,
           C = 2,
           D = 3,
           E = 4,
           F = 5,
           G = 6,
           H = 7;

reg [2:0] curr_state , nxt_state;

always @ (posedge clk)
begin
    if (rst)
        curr_state <= A;
    else
        curr_state<=nxt_state;
end

always @ (curr_state,datain)
begin
    case (curr_state)

        A:dataout <= 0;
        B:dataout <= 0;
        C:dataout <= 0;
        D:dataout <= 0;
    endcase
end

```

```

    E:dataout <= 0;
    F:dataout <= 0;
    G:dataout <= 0;
    H: if (datain == 1'b0)
        dataout <= 0;
        else if (datain == 1'b1)
            dataout <= 1;
        else
            dataout <= 0;
    endcase
end

always @ (datain,curr_state)
begin
    case (curr_state)
        A: if (datain == 0)
            nxt_state <= A;
            else if (datain == 1)
                nxt_state <= B;
            else
                nxt_state <= A;
        B:if (datain == 0)
            nxt_state <= C;
            else if (datain == 1)
                nxt_state <= B;
            else
                nxt_state <= A;
        C:if (datain == 0)
            nxt_state <= A;
            else if (datain == 1)
                nxt_state <= D;
            else
                nxt_state <= A;
        D:if (datain == 0)
            nxt_state <= C;
            else if (datain == 1)
                nxt_state <= E;
            else
                nxt_state <= A;
        E:if (datain == 0)
            nxt_state <= F;
            else if (datain == 1)
                nxt_state <= B;
            else
                nxt_state <= A;
        F:if (datain == 0)
            nxt_state <= A;
            else if (datain == 1)
                nxt_state <= G;
            else
                nxt_state <= A;
        G:if (datain == 0)
            nxt_state <= H;
            else if (datain == 1)

```

```

        nxt_state <= E;
    else
        nxt_state <= A;
    H: if (datain == 0)
        nxt_state <= A;
    else if (datain == 1)
        nxt_state <= D;
    else
        nxt_state <= A;
    endcase
    curr_state <= nxt_state;

end

endmodule

```

CLOCK DIVIDER BY (2, 4, 8, 16)

```

module clk_divider (clkkin , clk_2 , clk_4 , clk_8 , clk_16);

input clkkin;
output reg clk_2 , clk_4 , clk_8 , clk_16;

initial
begin
    clk_2 = 0;
    clk_4 = 0;
    clk_8 = 0;
    clk_16 = 0;
end

always @ (posedge clkkin)
clk_2 <= ~clk_2;



always @ (posedge clk_2)
clk_4 <= ~clk_4;

always @ (posedge clk_4)
clk_8 <= ~clk_8;

always @ (posedge clk_8)
clk_16 <= ~clk_16;

endmodule

```

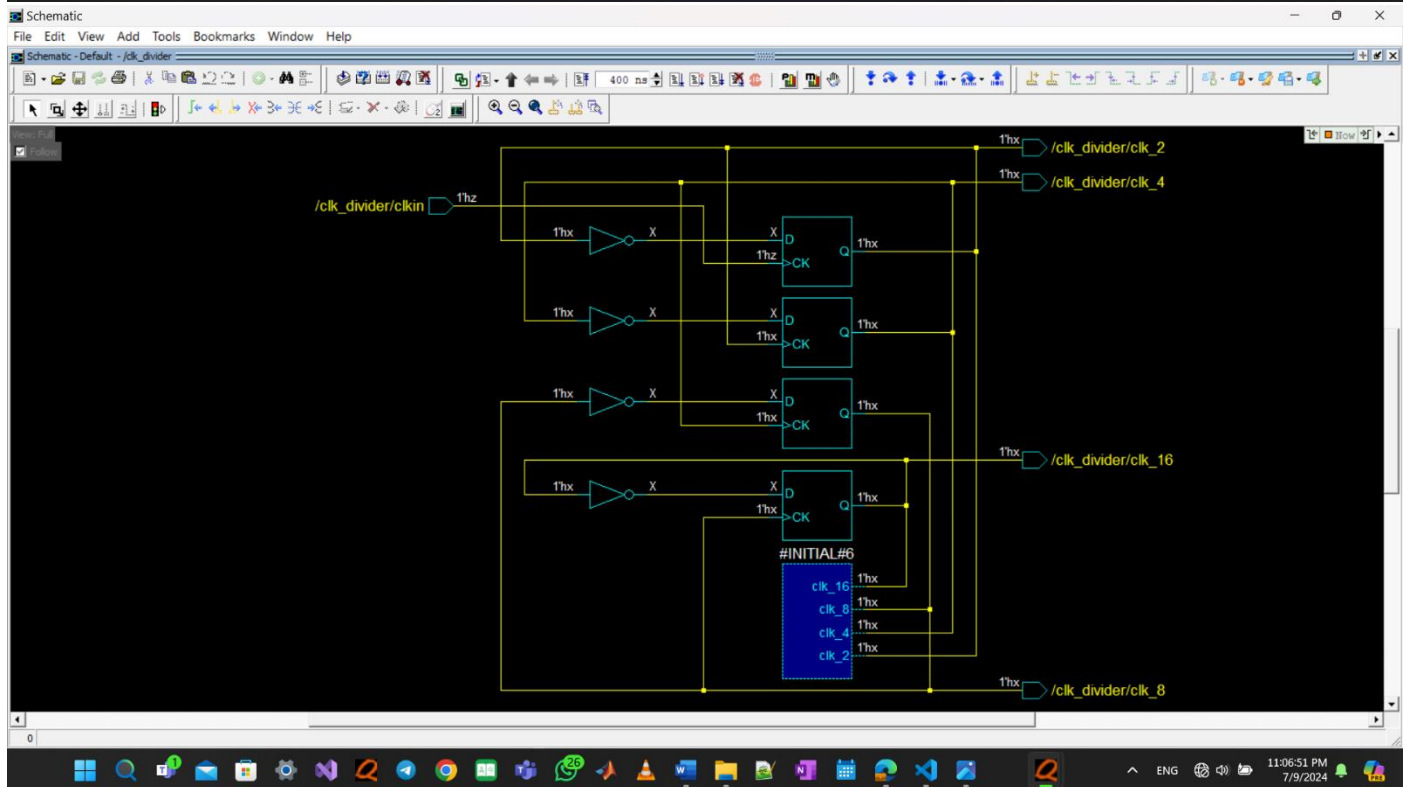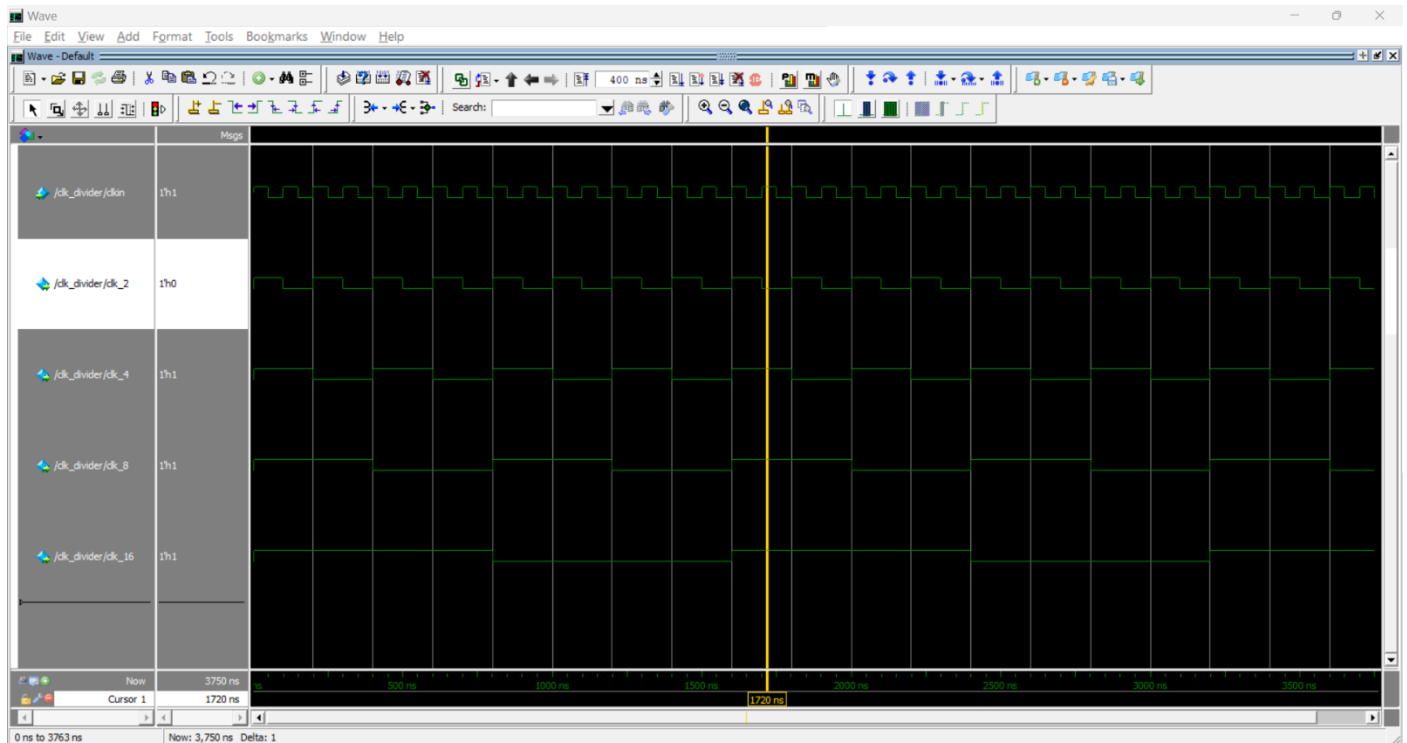

CLOCK DIVIDER BY 3

```
module clk_div_3 (clk_in , clkout);

input clk_in;
output reg clkout;

reg[1:0] edges_counts ;

initial
begin
edges_counts = 0;
```

```


    clkout =0;
end

always @(clkin)
    edges_counts <= edges_counts+1;

always @(*)
    begin
        if(edges_counts == 2'b11)
            begin
                clkout <= ~clkout;
                edges_counts = 0;
            end
        end
    end

endmodule

```

 

CLOCK DIVIDER BY 6

```

module clk_div_6 (rst , clkin , clkout);

input clkin,rst;
output reg clkout;

reg[2:0] edges_counts ;

always @(rst)
begin
    clkout = 0;
    edges_counts = 0;
end

```




```


always @(clk_in)
    if(~rst)
        edges_counts <= edges_counts+1;

always @(*)
    begin
        if(edges_counts == 3'b110)
            begin
                clk_out = ~clk_out;
                edges_counts = 0;
            end
        end
    end
end
endmodule

```

endmodule

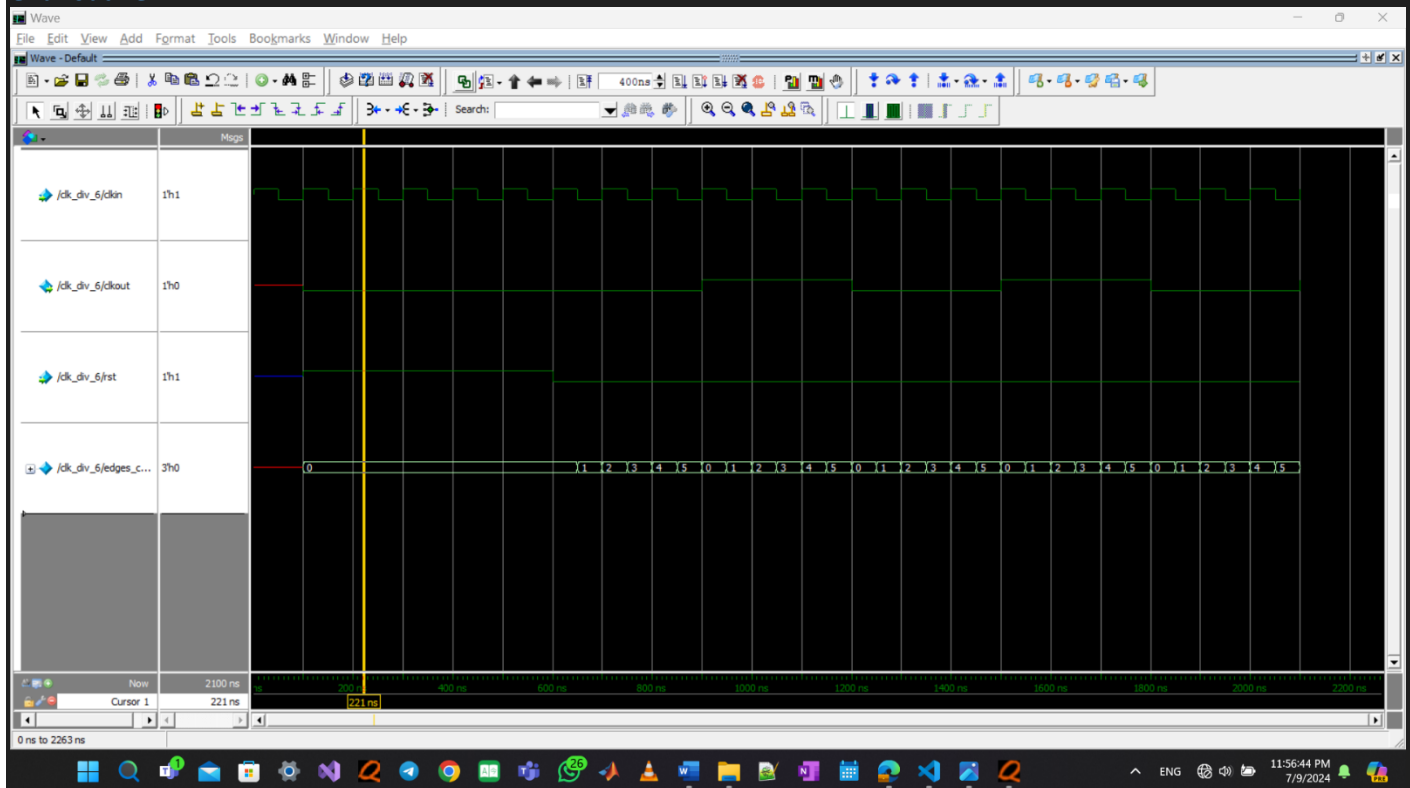

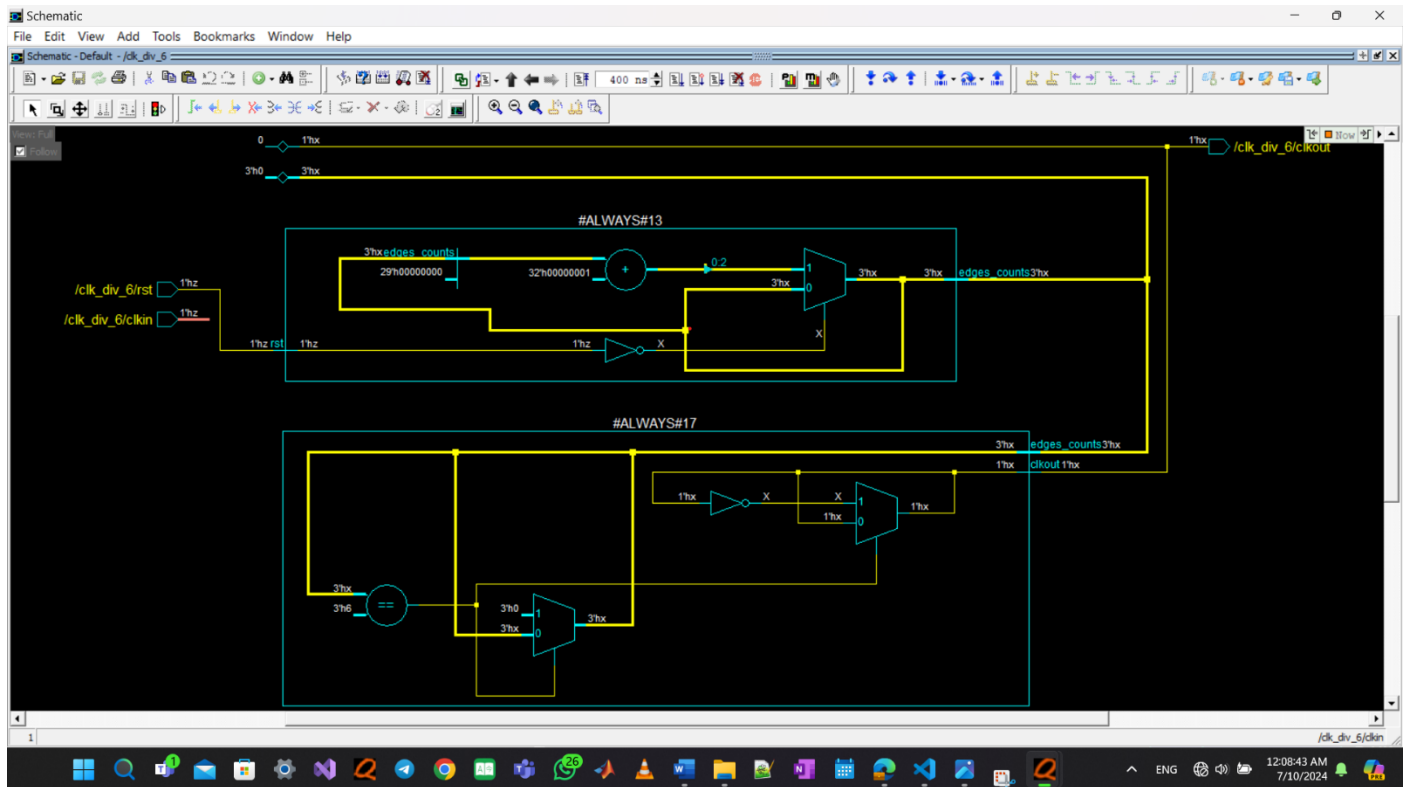

FIFO SYNCH

```

module synch_fifo (
    rest , clk , RE , WE , datain ,
    full_flag , empty_flag , dataout
);

input rest , clk , RE , WE ;
input [31:0] datain;
output reg full_flag , empty_flag;
output reg [31:0] dataout;

reg [31:0] mem [0:7];
reg [2:0] count;
reg [2:0] wptr;
reg [2:0] rptr;
reg empty;
reg full;

integer i;

always @(posedge clk , rest) begin
    if (rest)
        begin
            full_flag <= 1'b0;
            empty_flag <= 1'b1;
            dataout <= 'b0;
            count <= 'b0;
            empty <= 'b1;
            full <= 'b0;
            wptr <= 'b0;
            rptr <= 'b0;
        end
end

```

```

    for (i=0;i<8;i=i+1)      mem[i] <= 'b0;
end
else
begin
    if (WE && (count<8) && !(full))
    begin
        mem[wptr] <= datain;
        wptr <= wptr + 1;
        count <= count + 1;
        if(count == 3'b111)
        begin
            full_flag <= 1'b1;
            empty_flag <= 1'b0;
            empty <= 'b0;
            full <= 'b1;
        end
    end
    else
    begin
        full_flag <= 1'b0;
        empty_flag <= 1'b0;
        empty <= 'b0;
        full <= 'b0;
    end
end
else if (RE && (count>0) && !(empty))
begin
    dataout <= mem[rptr];
    rptr <= rptr + 1;
    count <= count - 1;
    if(count == 'b0)
    begin
        full_flag <= 1'b0;
        empty_flag <= 1'b1;
        empty <= 'b1;
        full <= 'b0;
    end
    else
    begin
        full_flag <= 1'b0;
        empty_flag <= 1'b0;
        empty <= 'b0;
        full <= 'b0;
    end
end
else
begin
    full_flag <= 1'b0;
    empty_flag <= 1'b1;
    dataout <= 'b0;
    count <= 'b0;
    empty <= 'b1;
    full <= 'b0;
    wptr <= 'b0;
    rptr <= 'b0;
end

```

```

        for (i=0;i<8;i=i+1)      mem[i] <= 'b0;
    end
end

end

endmodule

```

